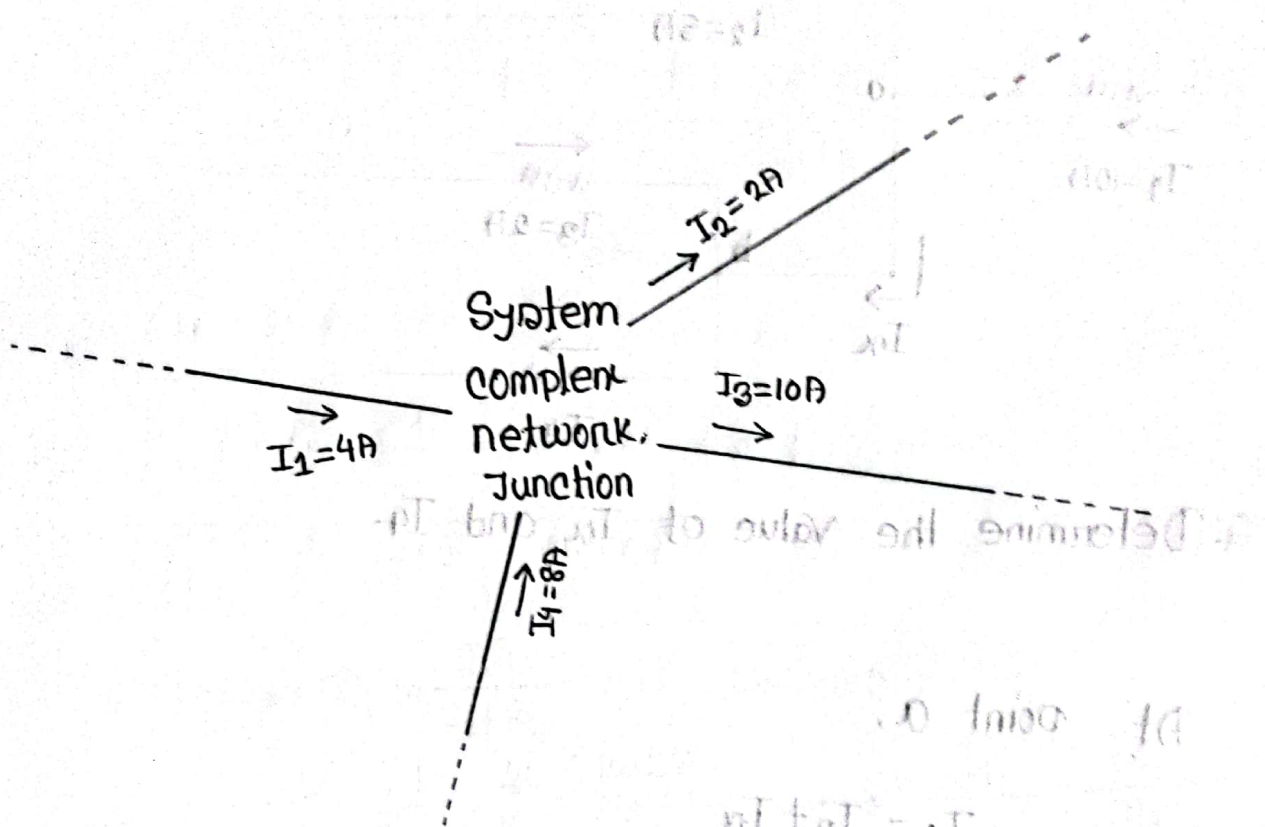


*** KCL:** The algebraic sum of the currents entering and leaving a junction of a network is zero.



In equation form, the above statement can be written as follows:

$$\sum I_{in} = \sum I_{out}$$


$\downarrow \qquad \downarrow$
 $I_1 \qquad I_2$

$$\Rightarrow I_1 + I_4 = I_2 + I_3$$

$$\Rightarrow 4A + 8A = 2A + 10A$$

$$\therefore 12A = 12A \text{ (check)}$$

Problem:

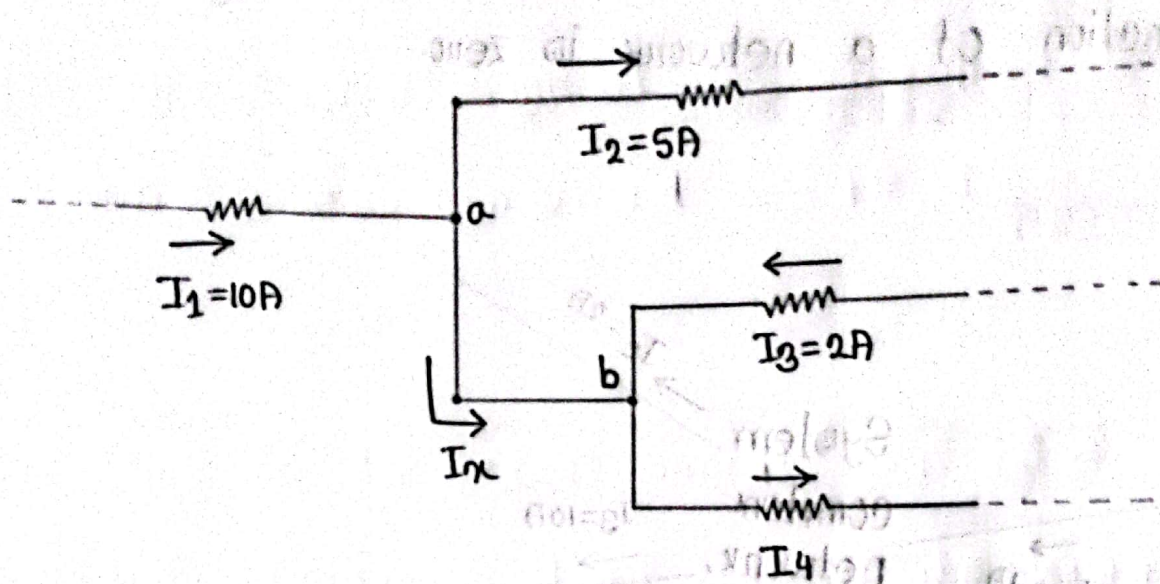

Q: Determine the value of I_x and I_4 .

Soln:

At point a,

$$I_1 = I_2 + I_x$$

$$\Rightarrow I_x = I_1 - I_2 = 10 - 5 = 5A$$

$$\therefore I_x = 5A$$

At point b,


$$I_4 = I_x + I_3$$

$$= 5A + 2A$$

$$= 7A$$

$$\therefore I_4 = 7A$$

Current Divider Rule: [CDR]

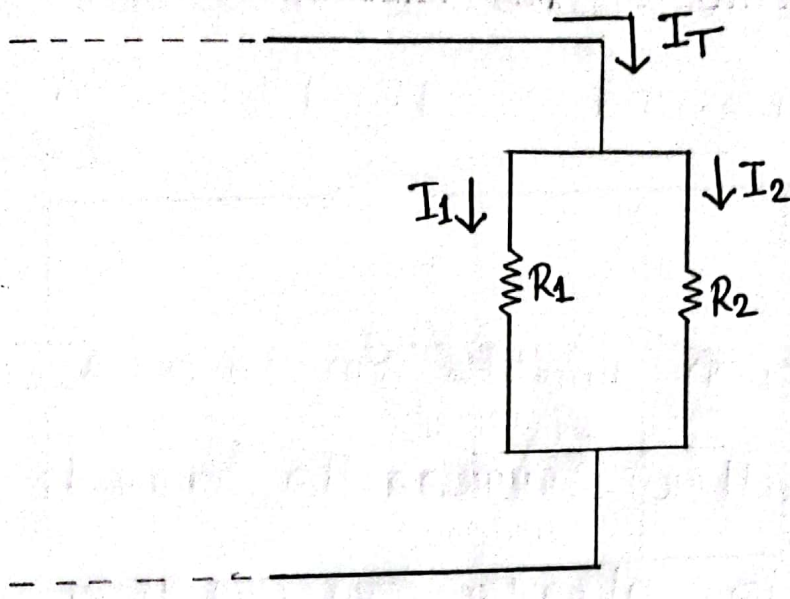

$$\rightarrow R_T = \frac{R_1 R_2}{R_1 + R_2}$$

* Ratio Rule:

$$\rightarrow \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$* I_1 = \frac{E}{R_1}$$


$$= \frac{I_T \times R_T}{R_1}$$

$$= \frac{I_T \left(\frac{R_1 R_2}{R_1 + R_2} \right)}{R_1}$$

$$\therefore I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I_T \quad **$$

$$\text{and } I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T \quad **$$

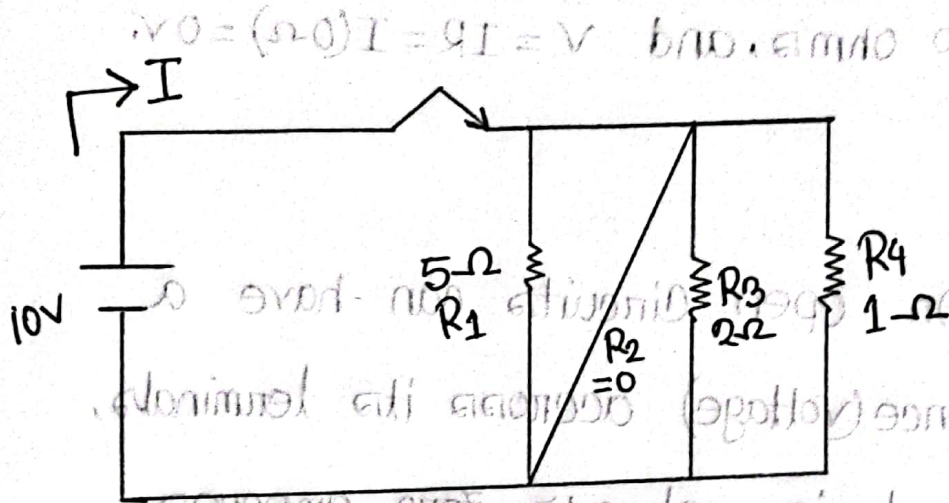☐ Short Circuit: A Short Circuit is a very low resistance, direct connection between two terminals of a network.



$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{0} + \frac{1}{2} + \frac{1}{1}$$

$$\Rightarrow \frac{1}{R_T} = \infty$$

$$\therefore R_T = 0 ; \frac{1}{\infty} = 0$$


$$\therefore I = \frac{E}{R} = \frac{10}{0} = \infty$$

↓
Shorted out

The current through the short circuit can be any value, as determined by the system it is connected to, but the voltage across the short circuit

is always zero volts because the resistance of the short circuit is assumed to be essentially zero ohms, and $V = IR = I(0\Omega) = 0V$.

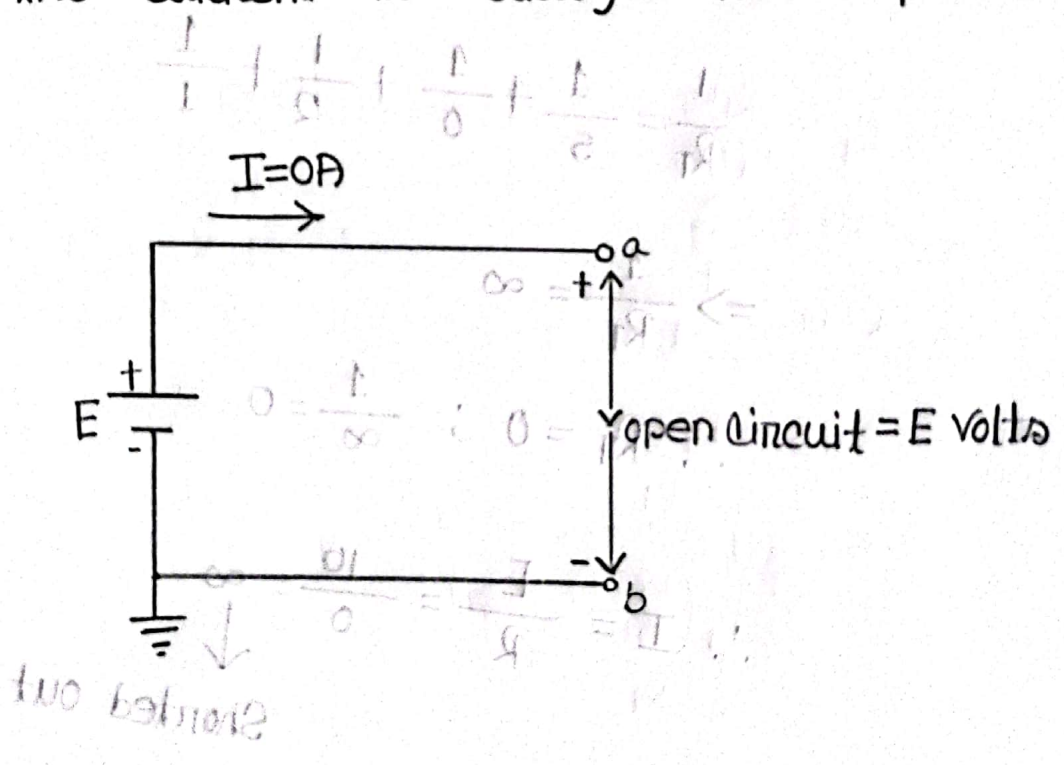Open Circuits: An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero amperes.




the current through the short circuit can be any value, as determined by the system it is connected to. But the voltage across the short circuit is always zero.

Chapter-7

Series-Parallel Circuit:


Reduce and Return Approach:

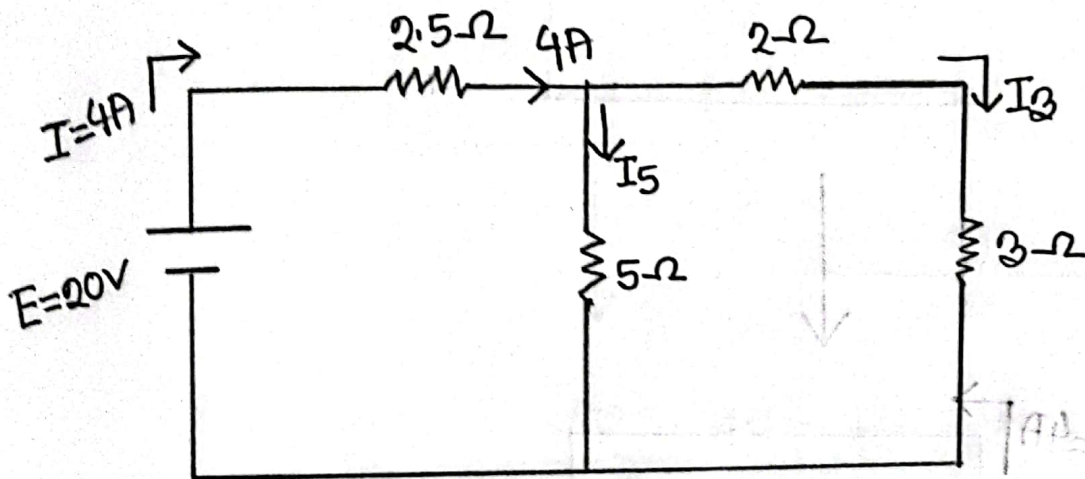

Find I_5 and I_3 .



Here, $R_T = 5\Omega$; $\begin{cases} R_S = 3 + 2 = 5\Omega \\ R_P = \frac{5 \times 5}{5 + 5} = \frac{25}{10} = 2.5\Omega \end{cases}$

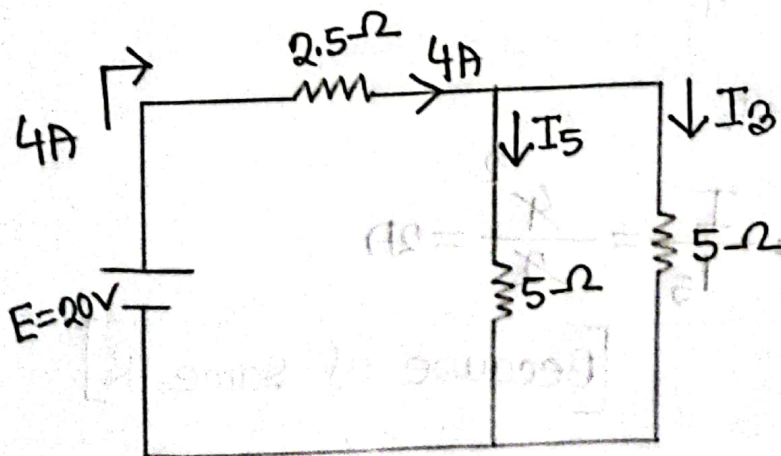$\therefore R_T = 2.5 + 2.5\Omega = 5\Omega$



$$\begin{aligned} * I_5 &= \frac{5}{5+5} \times I_T \\ &= \frac{5}{10} \times 4 \\ &= 2A \end{aligned}$$

$\therefore I_5 = 2A$

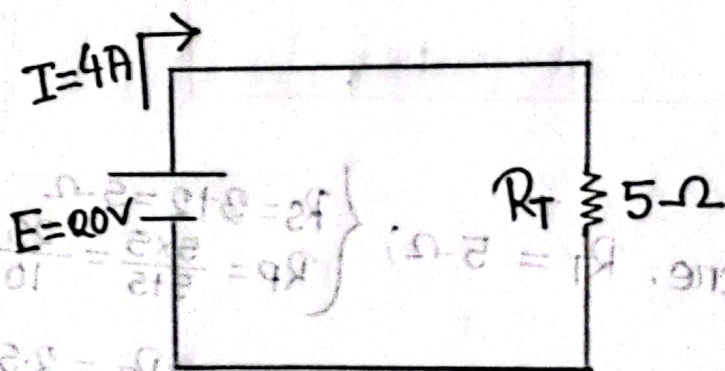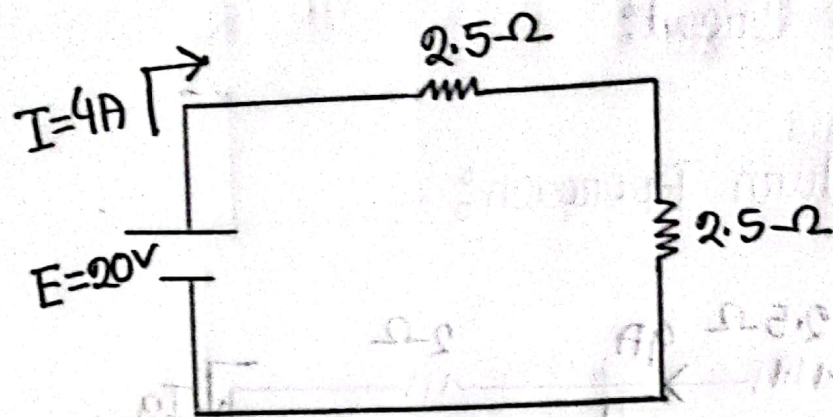



$$\bullet \quad I = \frac{E}{R_T} = \frac{20}{5} = 4A$$

$$\bullet \quad I_5 = 2A \downarrow$$


$$\therefore I_3 = \frac{I}{I_5} = \frac{4}{2} = 2A$$


[Because of same R]

▣ Ladder Network:

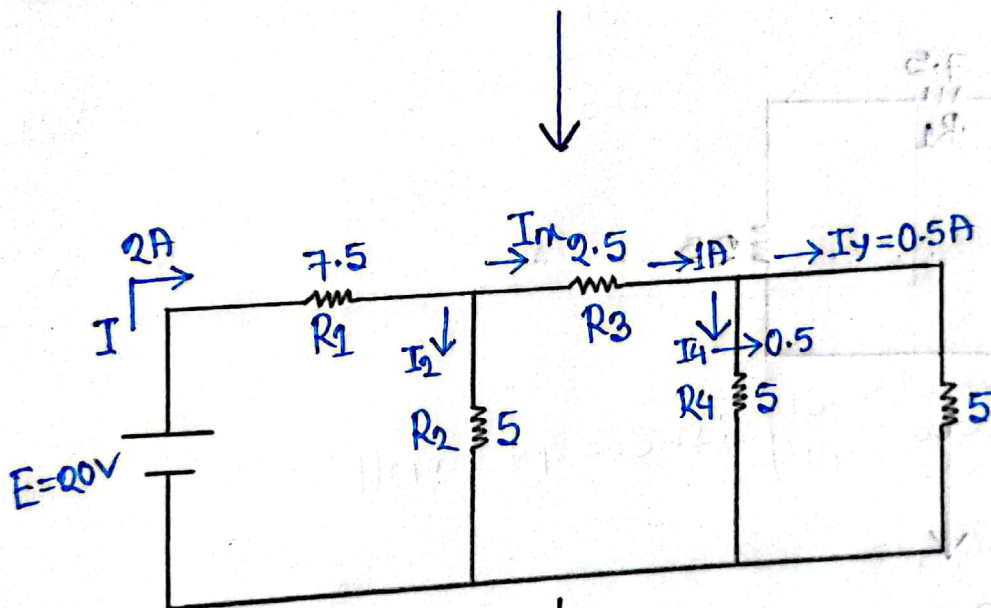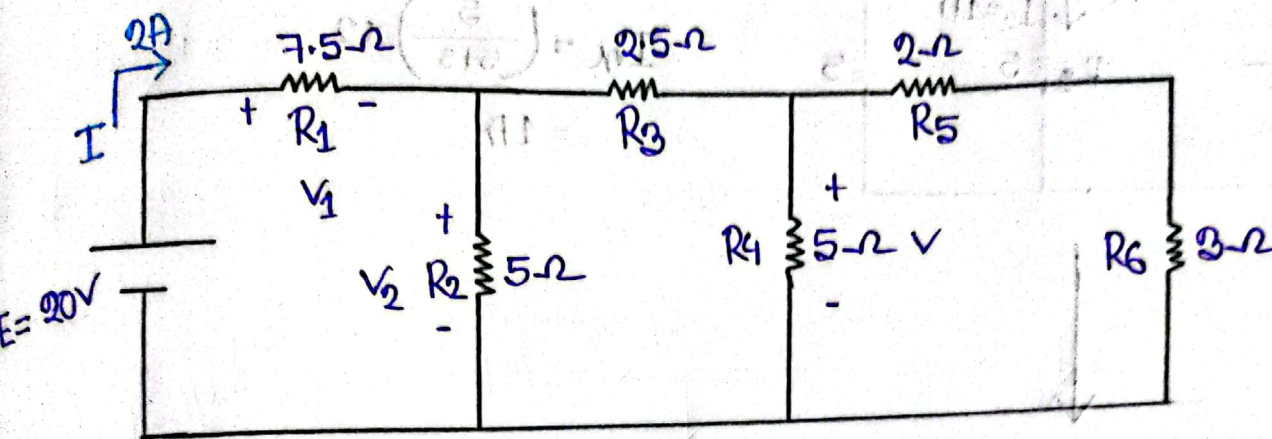


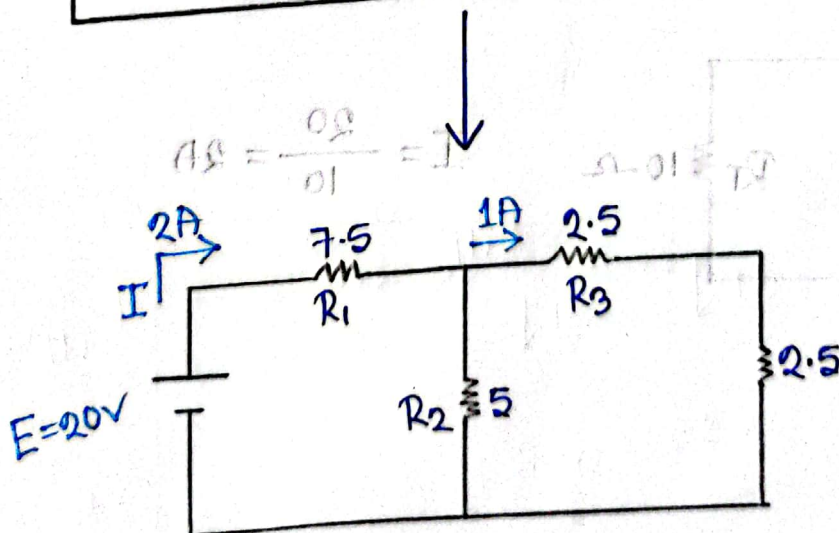
$$I_y = \left(\frac{5}{5+5} \right) \times 1 = 0.5A$$



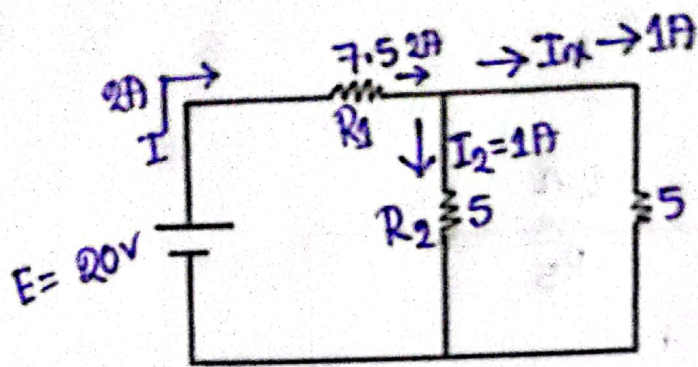

$$I_x = \left(\frac{5}{5+5} \right) \times 2$$

$$= 1A$$

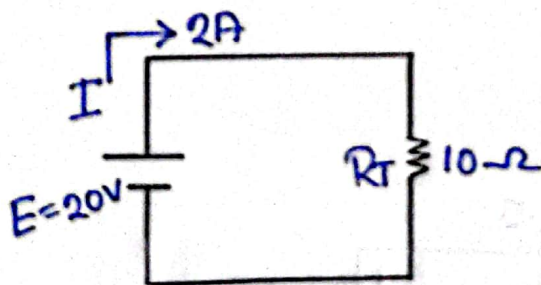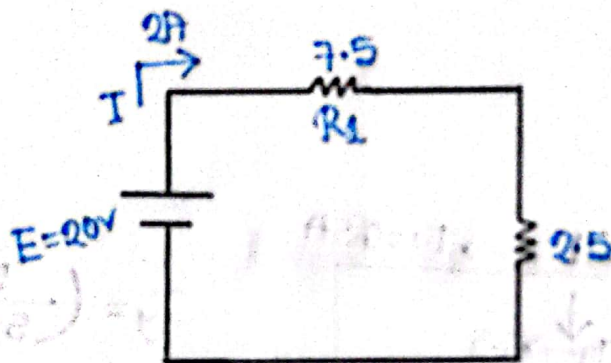

$$I = \frac{20}{10} = 2A$$