

## # Chapter-01:

### \* Units Measurement-

### \* System of Unit:

	M.K.S	C.G.S	F.P.S	SI
L →	m	c.m	ft	m
T →	sec.	Sec.	Sec	Sec
M →	kg	gm	lbnd	kg

### # Power of Ten:

$$10^1 = 10$$

$$10^2 = 100$$

$$10^3 = 1000 = \text{kilo}$$

$$= 1K$$

$$10^6 = 1000000 = 1 \text{ Mega} = 10^6 = 1M$$

$$10^9 = 1000000000 = 1 \text{ Giga} = 1G.$$

$$10^{12} = 1 \text{ tera}$$

$$= 1T$$

$$10^{18} = 1 \text{ exa}$$

$$= 1E$$

$$10^{15} = \text{peta} = 1P.$$

$$* 10^{-3} = \frac{1}{1000}$$

$$= 0.001 = 1 \text{ milli}$$

$$= 1 \text{ m}$$

$$10^{-6} = 1 \mu\text{.}$$

$$1 \mu\text{.} = 10^{-9}$$

$$10^{-12} = 1 \text{ pico}$$

$$1 \text{ Femto} = 10^{-15}$$

$$1 \text{ atto} = 10^{-18}$$

12

2.0.0

2.0.0

2.0.0

m

F

m.s

m

## = Conversion Between Power of Ten<sup>o</sup>

$$20,000 \text{ Hz} = ? \text{ MHz}$$

$$\begin{aligned} B &= 20 \times 10^3 \text{ Hz} \\ &= 20 \text{ KHz} = 0.02 \text{ MHz} \end{aligned}$$

$$0.01 \text{ ms} = ? \text{ } \mu\text{s}$$

$$\begin{aligned} &= 0.01 \times 10^{-3} \text{ s} = 0.01 \times 10^{-3} \times 10^{-3} \times 10^3 \text{ s} \\ &= 0.01 \times 1000 \times 10^{-6} \end{aligned}$$

$$\begin{aligned} &= 10^{-2} \times 10^3 \times 10^{-6} \text{ s} \\ &= 10 \times 10^{-6} \text{ s} \\ &= 10 \mu\text{s} \end{aligned}$$

$$1000 = 10^3$$

$$1000 = 10^3$$

## \* Atom:

### \* Voltage → Chapter-02

→ The simplest of all atoms is the hydrogen atom.

→ made up two basic particles, the proton and electron.

\* Atomic Structure: The atomic structure of any stable atom has an equal number of electrons and protons.

## ④ Materials:

\* Conductors: Less than 4 e<sup>-</sup> in outermost orbit

Examples: Al, Cu, etc.

\* Insulators: Greater than 4 e<sup>-</sup> in outermost Orbit.

Example: Ni.

\* Semi Conductor: Exactly 4 e<sup>-</sup> in outermost orbit.

Examples: Carbon, Silicon etc.

■ Some Good Conductors: Silver, Cu, Gold, Al, Fe, Steel, Brass.

metals

non metals

insulators

semiconductors

others


CamScanner

\* Voltage: It is the pressure from an electrical circuit's power source that pushes charged electrons (current) through a conducting loop, enabling them to do work such as illuminating a light.

\* an electromotive force or potential difference expressed in volts.

Equation:  $W = VQ$
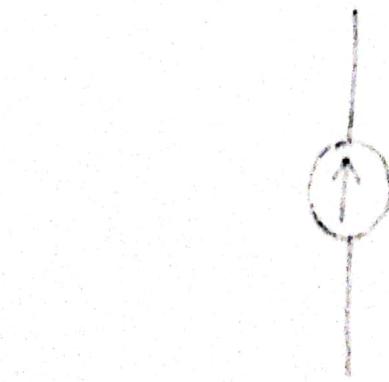
$$\Rightarrow V = \frac{W}{Q} ; = \frac{1J}{1C} = J\text{C}^{-1} = \text{volt} = V$$



source



metres








metres


Current: The current is a reaction to the applied voltage.

Equation: of math problems, good practice

$$\Rightarrow I = \frac{Q}{t}, r = \frac{1C}{1s} = 1\text{Amp.} = A.$$

## # Symbols:

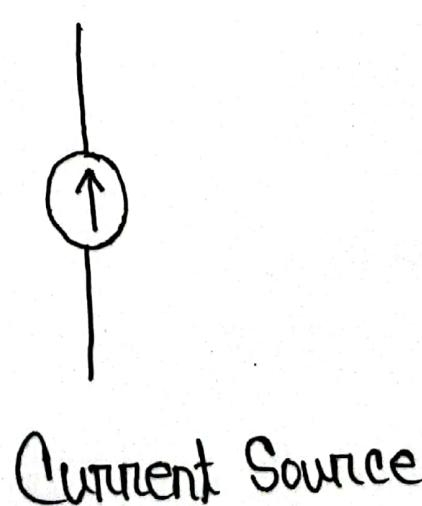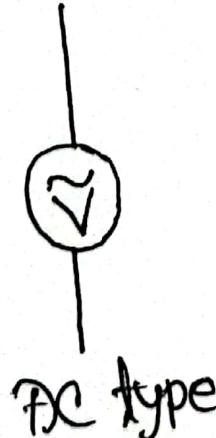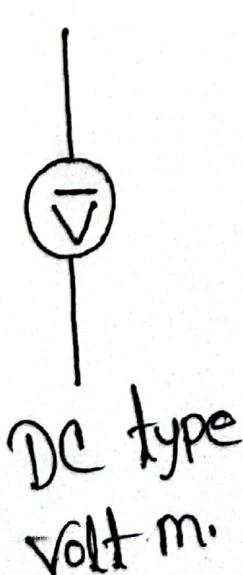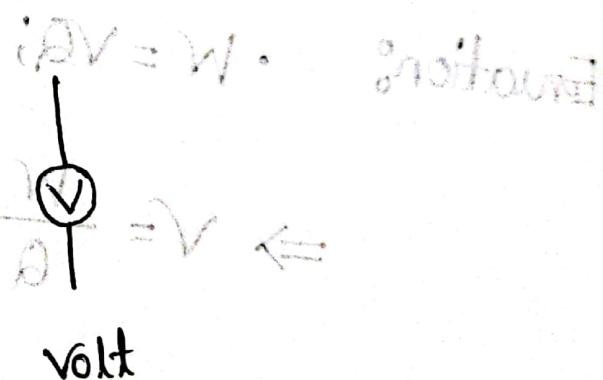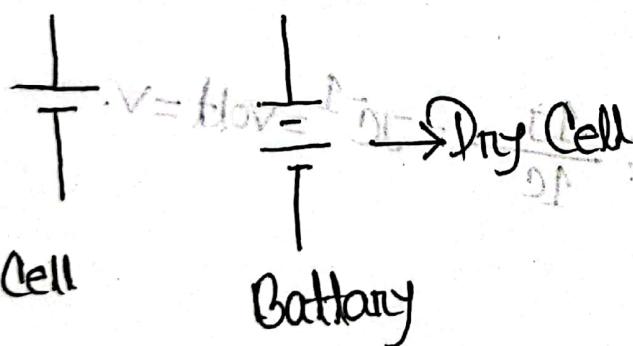

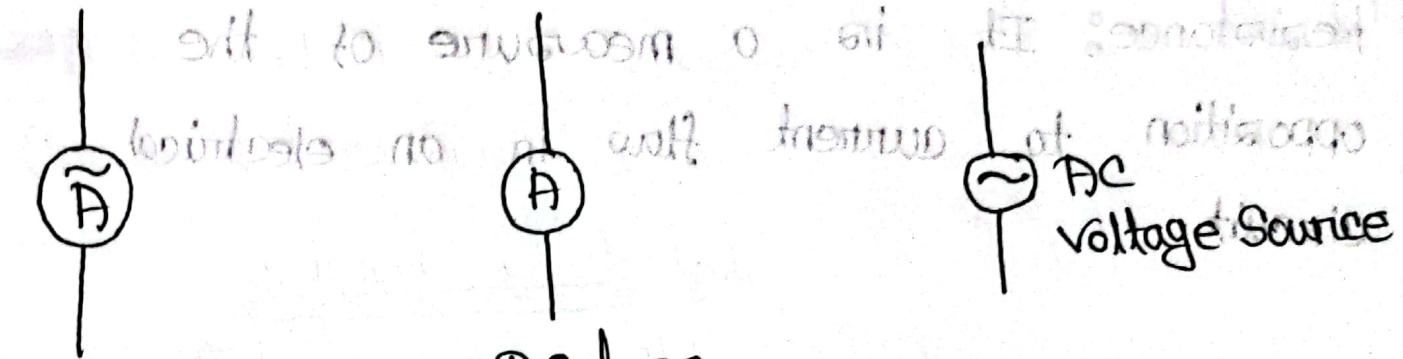

AC type  
Current Source

DC type  
Current Source

AC  
voltage Source

(indicated) direction. It

• Right.

• Cross-section view.

• Junction of two terminals.

• Indication  
;  $\rightarrow$  Left  
;  $\leftarrow$  Right

↑ R N D E S O

↑ R D E S O

↑ S O ;

# Resistance: It is a measure of the opposition to current flow in an electrical circuit.

### \* Dependency:

1. Material (Conductor)
2. Length.
3. Cross-sectional Area.
4. Temperature of the material.

1. Material:  $\xrightarrow{\text{Conductor}} R \propto L$ ;

2. Length:



$$\text{e} \rightarrow L_1 \quad R \uparrow$$

$$\text{e} \rightarrow L_2 \quad R \downarrow$$

$$\therefore R \propto L.$$

~~length~~



### 3. Cross-Sectional Area:

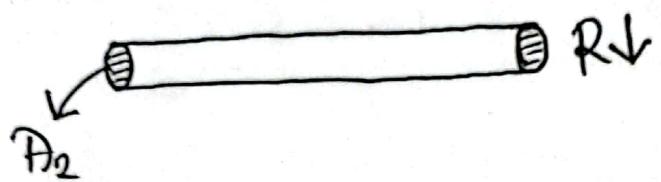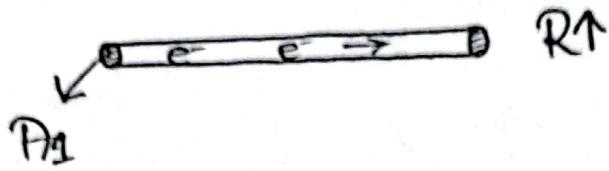



$$\therefore R \propto \frac{1}{A}$$

### 4. Temperature:

For  $\rightarrow$  Conductor

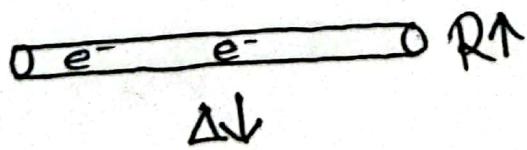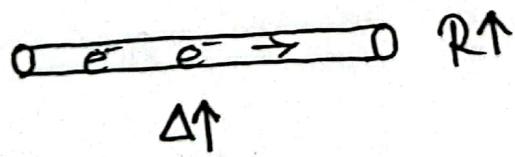

Semi-Conductor:

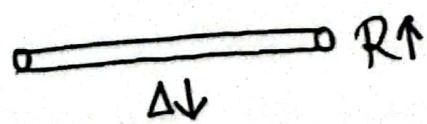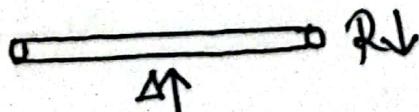


# Equations:

$$R \propto \frac{L}{A}$$

$$\Rightarrow R = \rho \frac{L}{A};$$

Symbols:

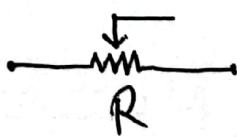


$$\frac{L}{A} \propto \rho$$

Because

proportional  $\leftarrow \text{not}$



ΔA

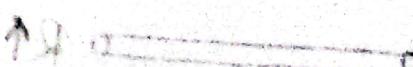

ΔA





ΔA

Because

## Chapter-1

### Ohm's Law, Power and Energy

# Ohm's Law:

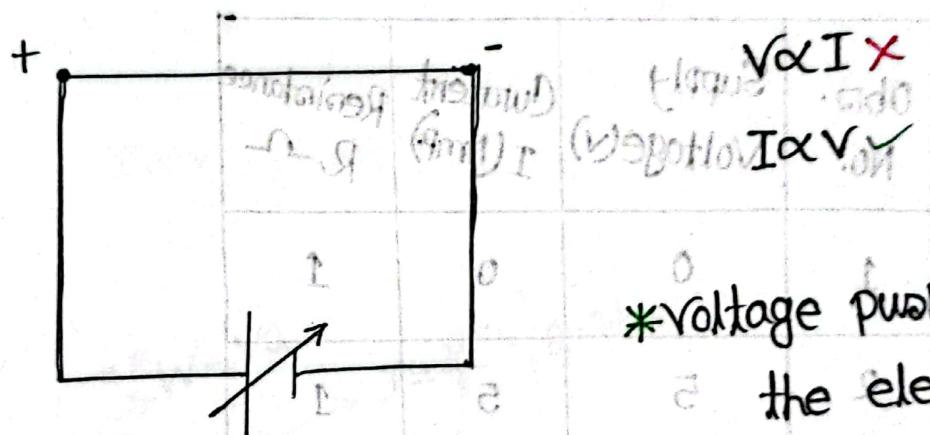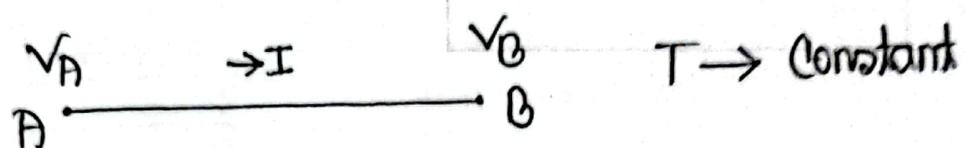

$$V_{AB} = V_A - V_B \quad [V_A > V_B]$$

$$\Rightarrow I \propto V_A - V_B$$


$$\Rightarrow I \propto V$$

$$\Rightarrow I = GV ; R = \frac{1}{G}$$


$$= \frac{1}{R} V$$

\*  $I$  = Intensity of current

$$\therefore V = IR$$

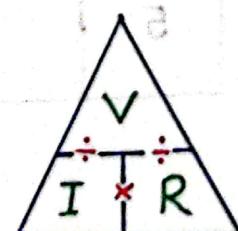

# # Examination of Ohm's Law:

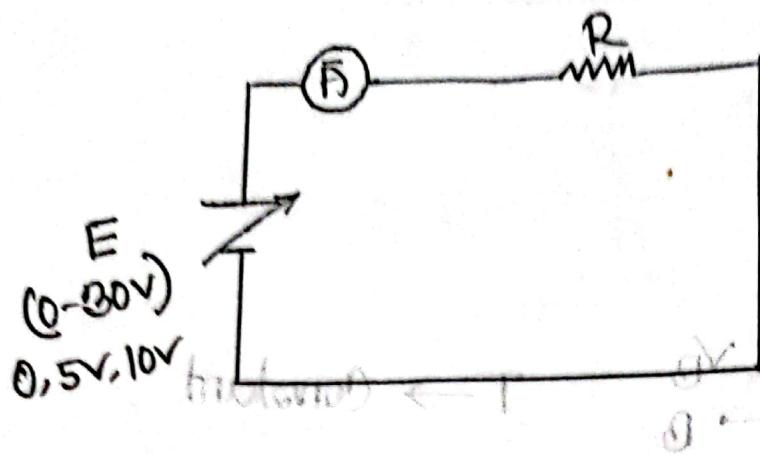


T-constant

Obs. No.	Supply Voltage(V)	Current I(AMP)	Resistance R, $\Omega$
1	0	0	1
2	5	5	1
3	10	10	1
4	15	15	1
5	20	20	1

$$V = IR$$

$$\Rightarrow I = \frac{V}{R}$$

## # Verification of $I \propto V$ :

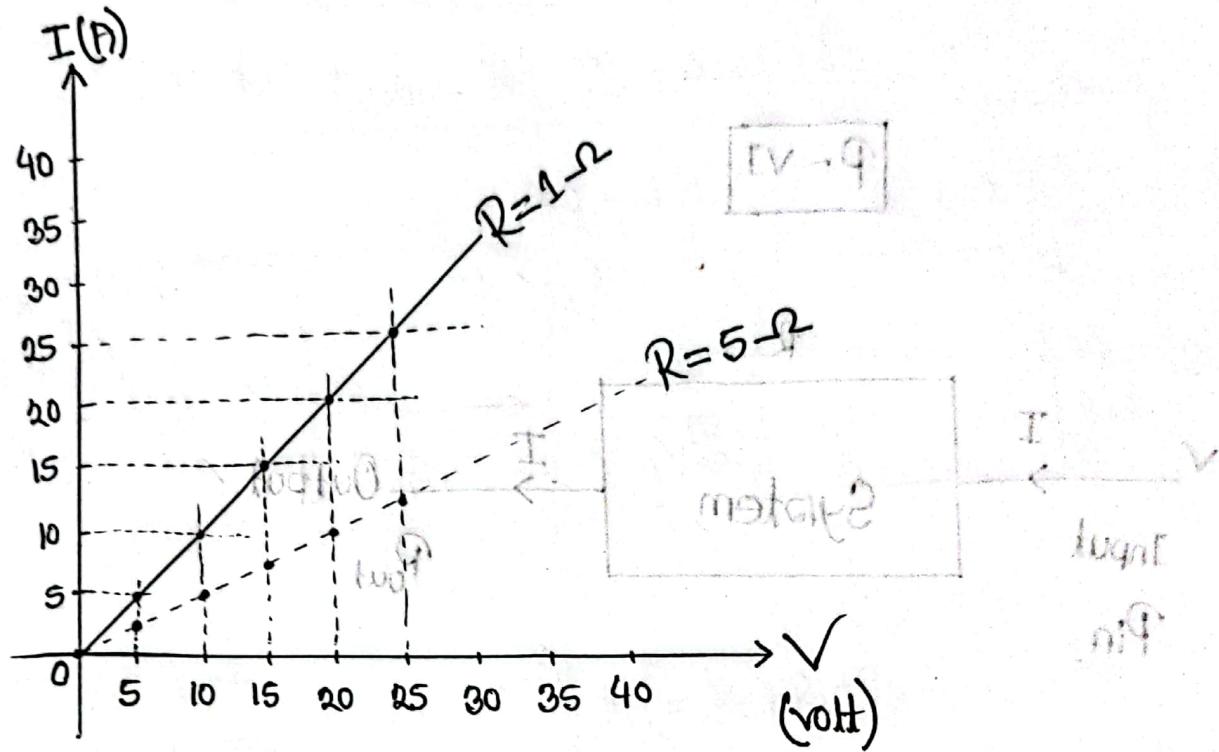

$I \propto V \rightarrow \text{Verified}$

## # Power:

$$** W = Pt$$

$$P = \frac{W}{t} = \frac{V \cdot Q}{t} \stackrel{* * W = VA}{=} VI = IRI = I^2 R = \frac{V^2}{R} \cdot R = \frac{V^2}{R}$$


$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

# Efficiency:  $\eta$

$$P = VI$$

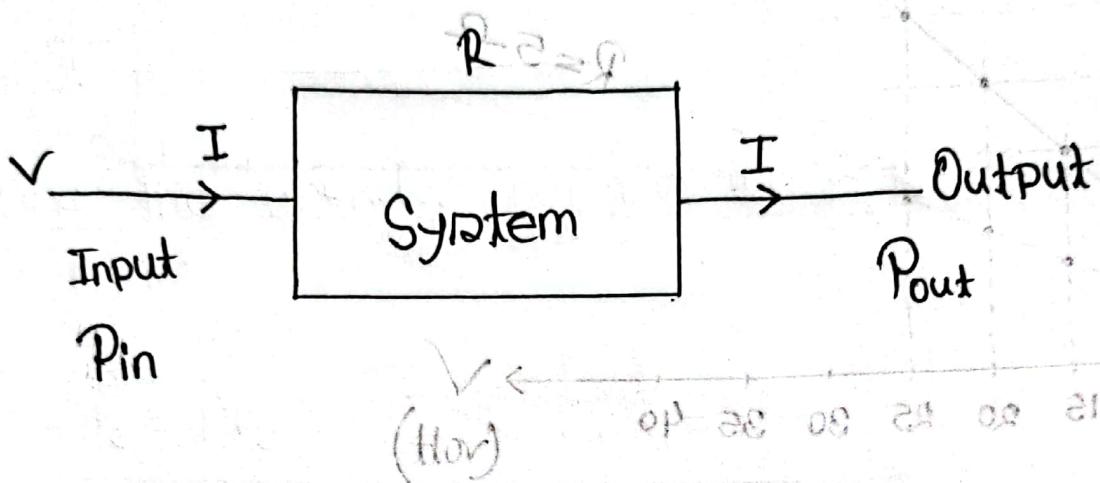

$$\eta = \frac{\text{Output}}{\text{Input}}$$



$$= \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$= \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

$$W = P \cdot t$$

## Chapter-5

### Series DC Circuits

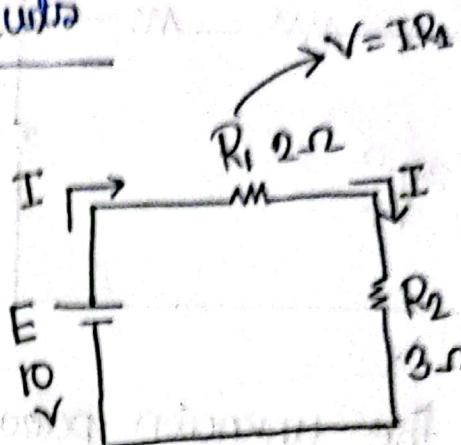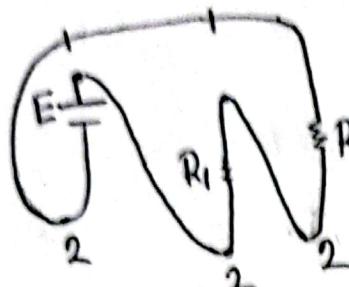

Series

\* Series ৰ মধ্যে Same  
Current flow হ'ব।

$$R_s = R_1 + R_2 + R_3 + \dots + R_n$$

$$\begin{aligned} R_s &= N \cdot R \rightarrow R_t = R_1 + R_2 + R_3 \\ &= 3R [\because R = R_1 = R_2 = R_3] \\ &= N \cdot R [\text{No. of Resistor}] \end{aligned}$$

$V = IR$  Main Current


$$\therefore R_t = N \cdot R$$

$$\therefore V_1 = IR_1 = 2 \times 3 = 6V$$

$$\therefore V_2 = IR_2 = 2 \times 2 = 4V$$

$$\therefore V_3 = IR_3 = 5 \times 2 = 10V$$
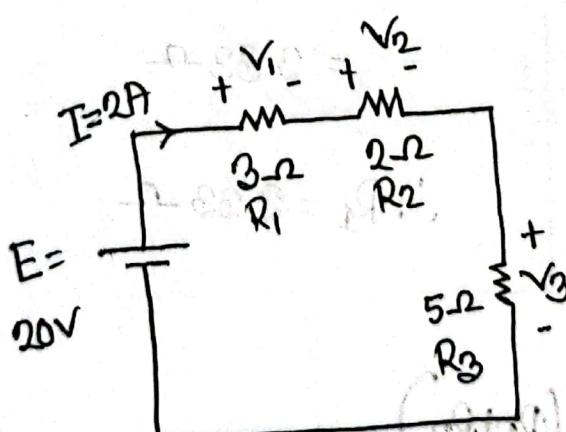
$$\begin{aligned} I &= \frac{E}{R_t} \\ &= \frac{20}{10} \\ &= 2A \end{aligned}$$



$$\therefore R_t = 3 + 2 + 5 = 10\Omega$$

#  $P = VI$  :  $P = P_1 + P_2 + P_3 + \dots$

$$P_1 = V_1 I = 6 \times 2 = 12W$$


$$P_3 = V_3 I = 10 \times 2 = 20W$$

$$P_2 = V_2 I = 4 \times 2 = 8W$$

$$P = VI = 20 \times 2 = 40W$$

$P = VI$

Example: 5.7

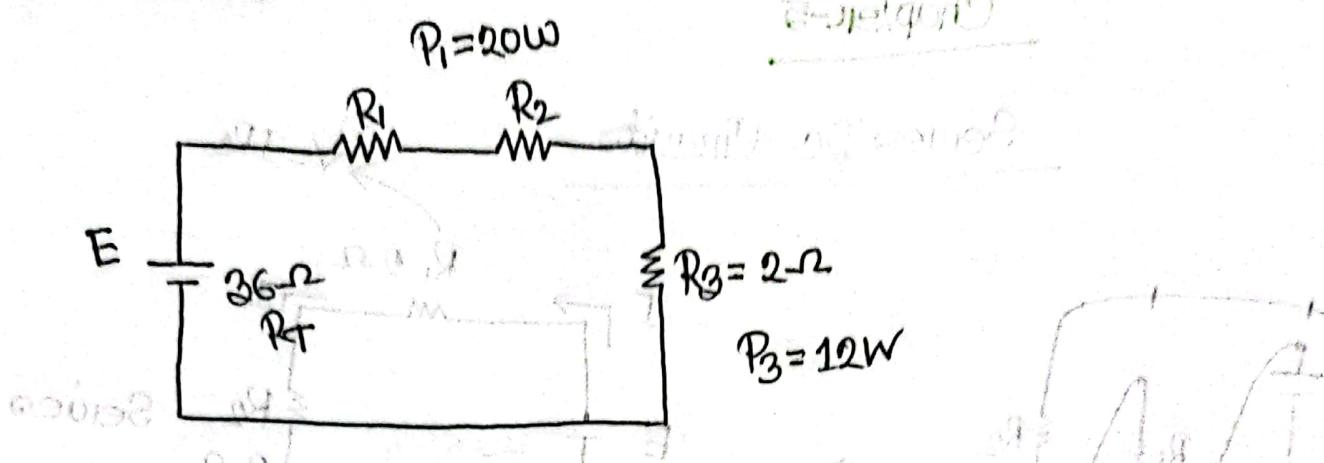

Find the unknown parameters  $R_1, R_2, E, I$ .

Sol<sup>n</sup>:

$$P_3 = I^2 R_3 \Rightarrow P_3 = I^2 \cdot 2 \Rightarrow P_3 = I^2 R_1$$

$$\Rightarrow I^2 = \frac{P_3}{R_3} = \frac{12}{2} \Rightarrow R_1 = \frac{P_1}{I^2}$$

$$I = \frac{12}{2} A = \frac{20}{6} \Omega$$

$$\therefore I = \sqrt{6} A = 2.45 A$$

$$= 3.33 \Omega$$

$$\therefore R_1 = 3.33 \Omega$$

$$\therefore R_2 = R_T - (R_1 + R_3)$$

$$= 36 - (3.33 + 2)$$

$$\therefore E = I R_T$$

$$= 2.45 \times 36$$

$$= 86.67 \Omega$$

$$\therefore E = 86.161 V$$

$$P = EI = 86.161 \times 2.45$$

$$= 216.09 W$$

$$P = P_1 + P_2 + P_3 = 216.09 W$$


## Kirchhoff's Theory

$$\sum V_c = 0$$


$$\Rightarrow +V + (-V_1) + (-V_2) + (-V_3) = 0$$

$$\Rightarrow V = V_1 + V_2 + V_3$$
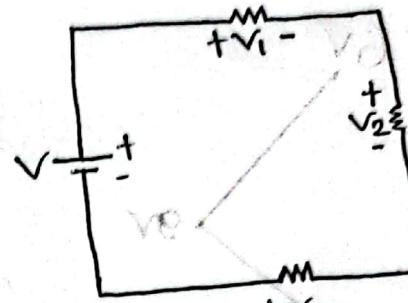
$$\Rightarrow V_{\text{ruler}} = V_{\text{drop}} \quad (i)$$



## KVL

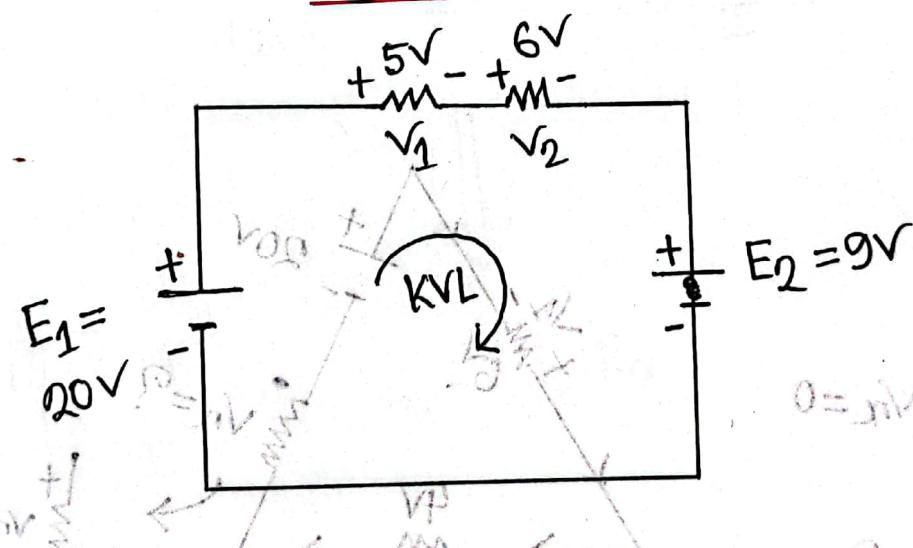



$$\sum V_c = 0$$

$$\Rightarrow +E_1 + (-V_1) + (-V_2) + (-E_2) = 0$$

$$\Rightarrow E_1 - V_1 - V_2 - E_2 = 0$$

$$\Rightarrow 20 - V_1 - 6 - 9 = 0$$

$$\Rightarrow V_1 = 5V$$

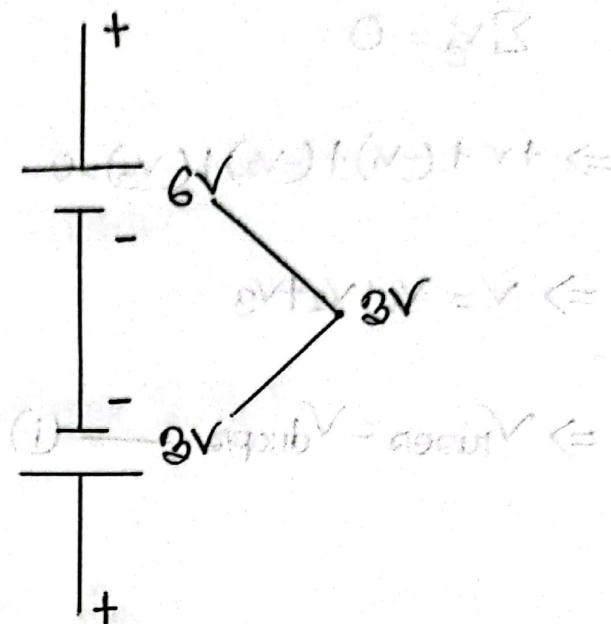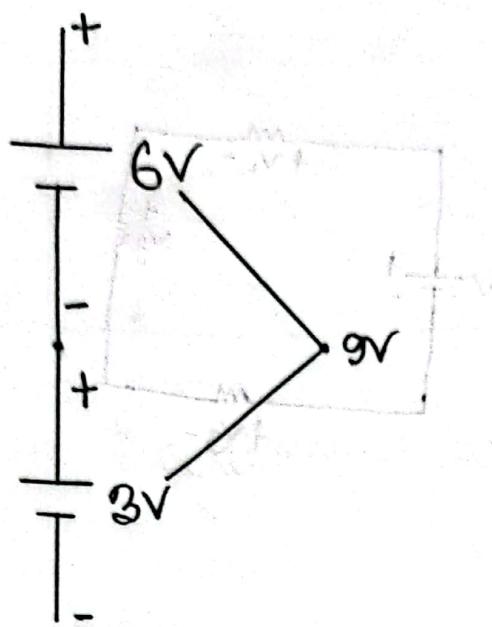

### Problem - 2°

F.

$$\sum V_x = 0$$

$$\Rightarrow +20V + V_1 - V_2 + V_{Rx} = 0$$


$$\Rightarrow 20 + 6 - 4 + V_{Rx} = 0 \quad \text{---} \quad \Theta$$

$$\Rightarrow V_{Rx} = -22V$$


$\Rightarrow -V_{Rx} = 22V$  but  $V_{Rx}$  can't be negative; So we have

$\therefore V_{Rx} = 22V$  to define it correctly

$$\text{So, } V_{Rx} = 22V$$

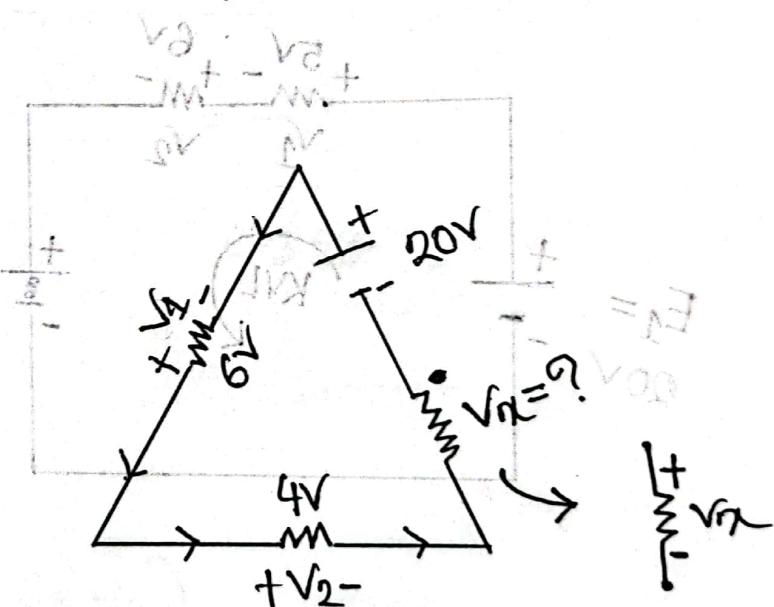

由VDR (Voltage Divider Rule):

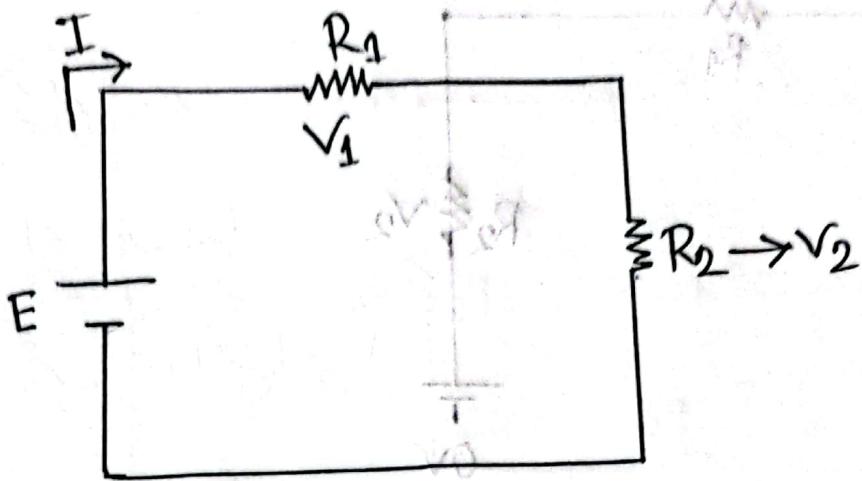

$$\rightarrow V_1 = IR_1$$


$$\rightarrow V_2 = IR_2$$

$$\Rightarrow V_1 = \left(\frac{E}{R_T}\right) R_1$$

$$\Rightarrow V_2 = \left(\frac{E}{R_T}\right) R_2$$

$$\begin{matrix} \uparrow \\ I \end{matrix}$$

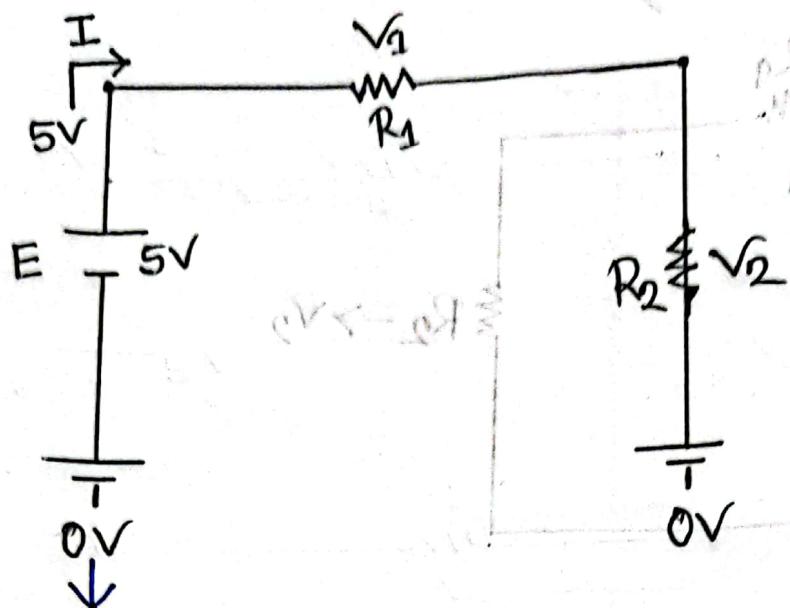由  $V_x = \left(\frac{E}{R_T}\right) R_x$




Ground  
voltage

$$\text{IR} = \text{AV} \leftarrow$$

$$\text{IR} = \text{IV} \leftarrow$$

$$R\left(\frac{E}{R_1}\right) = \text{AV} \leftarrow$$

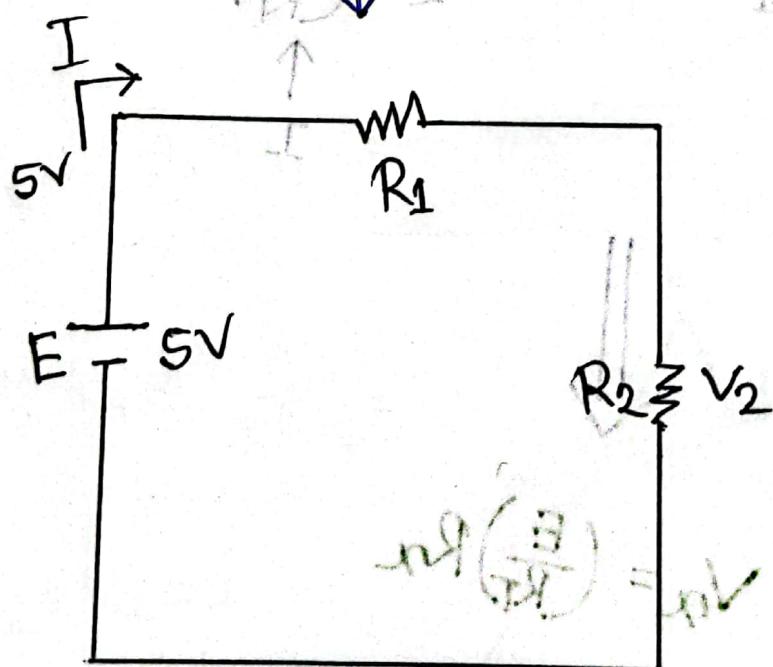
$$R\left(\frac{E}{R_1}\right) = \text{IV} \leftarrow$$



$$R\left(\frac{E}{R_1}\right) = \text{AV}$$




AV

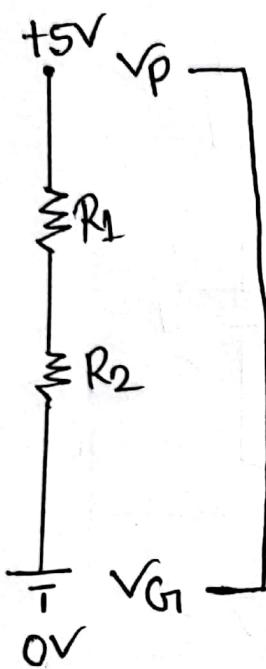Point Voltage: From the point to ground voltage.





$$\begin{aligned}V &= V_P - V_{G1} \\&= 5 - 0 \\&= 5 \text{ V}\end{aligned}$$

$$5\text{V} + 0\text{V} = 5\text{V}$$

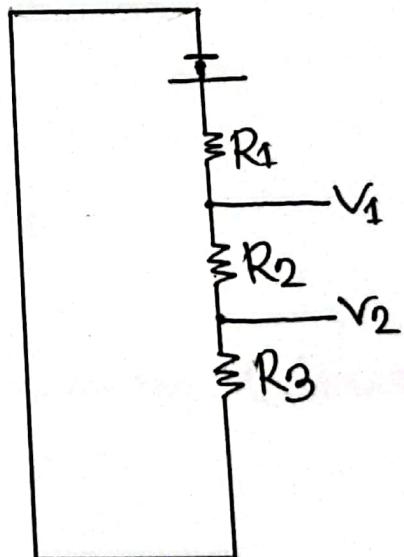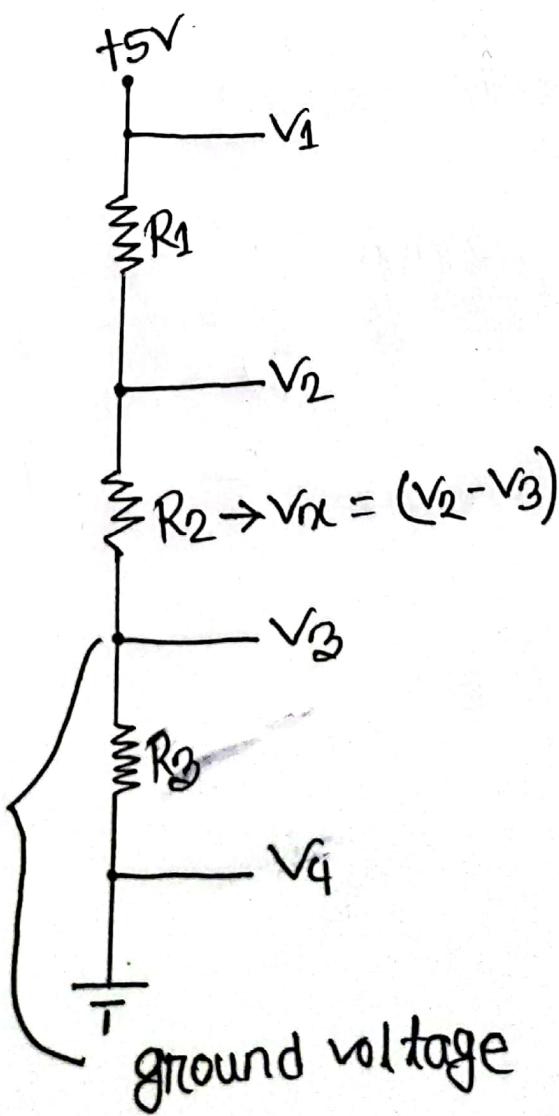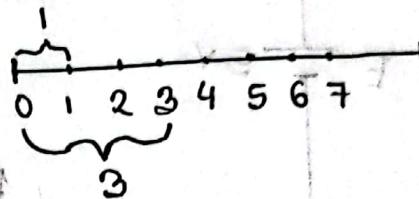


Bottom drawing of knot out

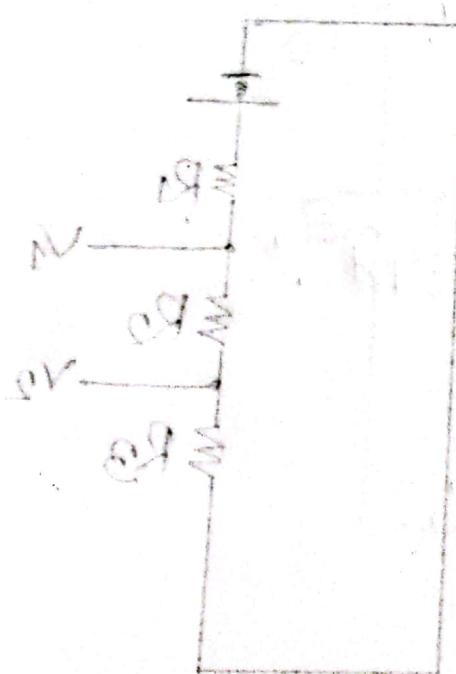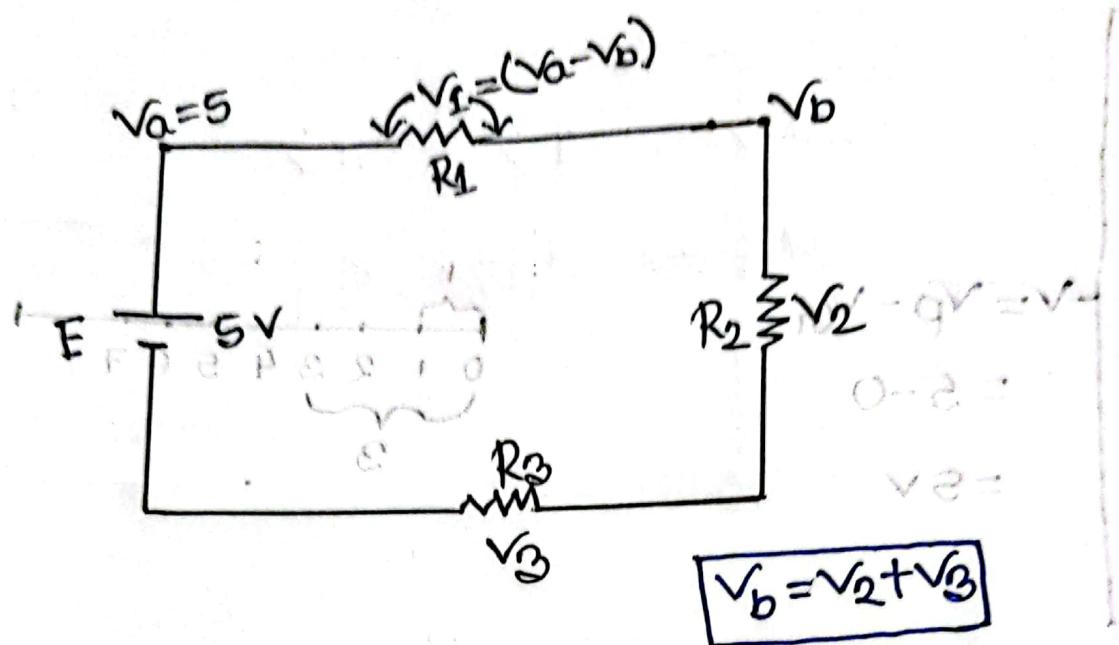

$$(EV - EV) = EV \leftarrow$$

## ④ Parallel DC Circuits

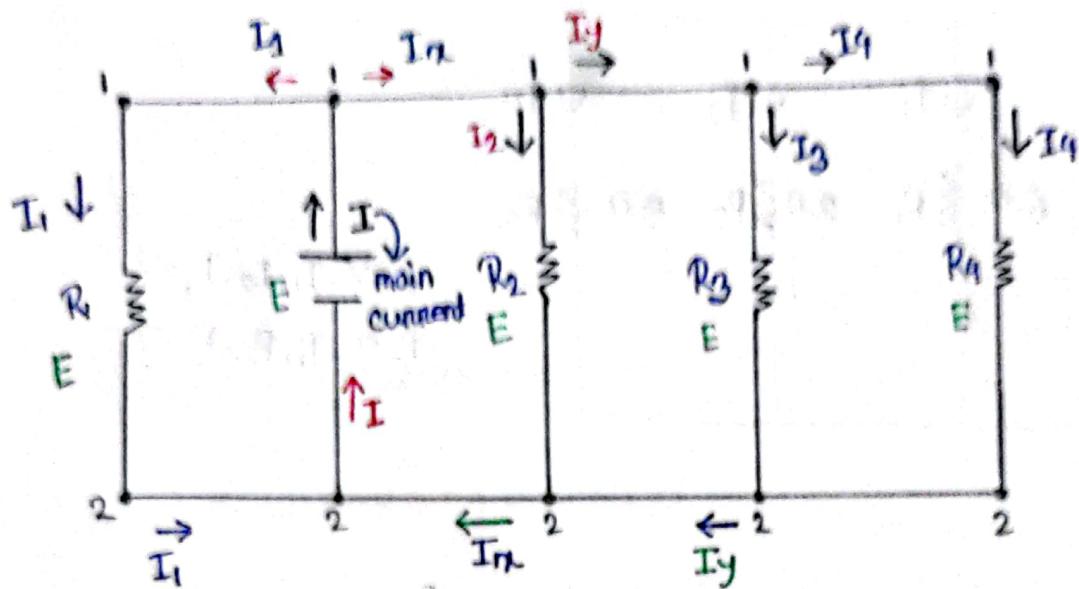

Note: \* Parallel Circuit: Voltage Same.


\* Series Circuit: Current Same.

$$\boxed{\text{□}} \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots + \frac{1}{R_n}$$

\* 2<sup>nd</sup> Resistance:  $R_T = \frac{R_1 R_2}{R_1 + R_2} \rightarrow \text{for 2 Resistance}$

$$\boxed{\text{□}} \quad I = \frac{E}{R_T}; \quad P = VI = I^2 R$$

## Problem:

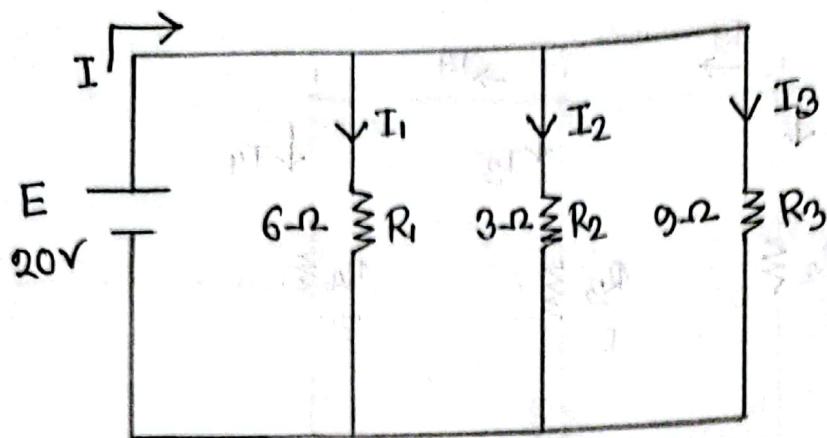

$I = ?$ ,  $I_1, I_2, I_3 = ?$   
 $P = ?$ ,  $P_1, P_2, P_3 = ?$

Sol<sup>n</sup>:

Here,

$$R_{T_1} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{6+3} = \frac{18}{9} = 2\Omega$$

$$\therefore R_{T_1} = 2\Omega$$

$$\therefore R_T = \frac{R_{T_1} R_3}{R_{T_1} + R_3} = \frac{2 \times 9}{9+2} = \frac{18}{11} = 1.64\Omega$$

$$\therefore R_T = 1.64\Omega$$

$$\therefore I = \frac{E}{R_T} = \frac{20}{1.64} = 12.22A$$

$$I_1 = \frac{E}{R_1} = \frac{20}{6} = 3.33A$$

$$I_2 = \frac{E}{R_2} = \frac{20}{3} = 6.67A$$

$$I_3 = \frac{E}{R_3} = \frac{20}{9} = 2.22A$$

$$\begin{aligned}I &= I_1 + I_2 + I_3 \\&= 3.33 + 6.67 + 2.22 \\&= 12.22 \text{ A}\end{aligned}$$

$$P_1 = VI_1 = 20 \times 3.33 = 66.6 \text{ W}$$

$$P_2 = VI_2 = 20 \times 6.67 = 133.4 \text{ W}$$

$$P_3 = VI_3 = 20 \times 2.22 = 44.4 \text{ W}$$

$$\therefore P = VI = 20 \times 12.22 = 244.4 \text{ W}$$

OR

$$\begin{aligned}P &= P_1 + P_2 + P_3 \\&= 66.6 + 133.4 + 44.4 \\&= 244.4 \text{ W}\end{aligned}$$

Note: Series and Parallel Circuit have same power